

digi
MENTO
EDUCATING ON GO...

DIGITAL LOGIC

WorkBook

2018

DigiMento Educational Service Pvt. Ltd.

Q1. $(673.23)_{10}$ convert this decimal number into octal number system?

Note : Convert till 4 decimal positions. Ex: if your answer is 6565.414687.

Write answer as 6565.4146

Q2. Duality of the function $F = X'YZ + XY' + YZ'$

a. $(X+Y'+Z).(X'+Y).(Y+Z')$

b. $(X'+Y+Z).(X+Y).(Y+Z')$

c. $(X'+Y+Z).(X+Y).(Y+Z)$

d. None of these

Q3. If number of one's even then EX OR output?

Q4. The maximum no of self-dual functions with 3 Boolean variables is?

a. 32


b. 256

c. 16

d. None of these

Q5.

The output of X is a. $A'C+AB$

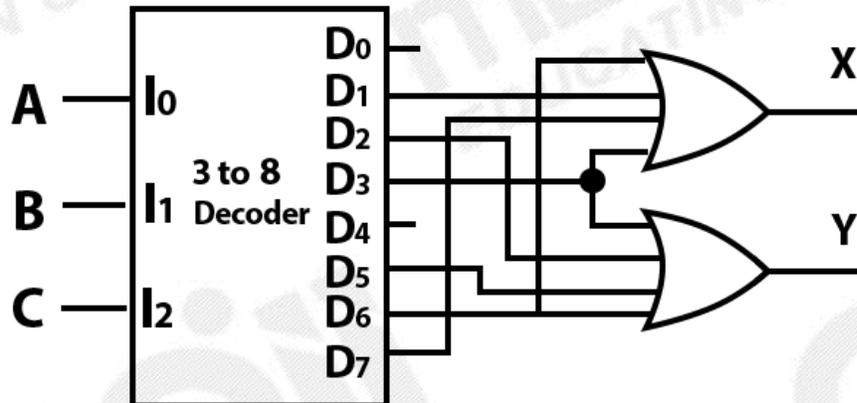


- a. $A'C+AB$
- b. $AC'+BC$
- c. $AC+BC$
- d. $AC'+BC'$

Q6.

The output of Y is

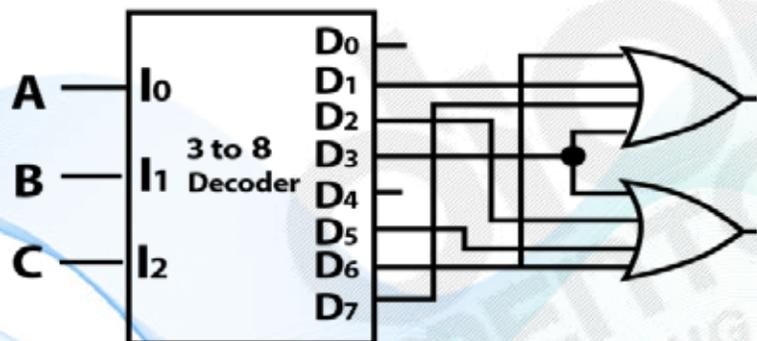
- a. $A'B+BC'+A'B'C$
- b. $BC'+BA+AB'C$
- c. $BC'+BA'+CB'A$
- d. None of these




Q7. Consider the given XY flip-flop

What values of X, Y respectively put flip flop in SET mode?

- a. 0, 0
- b. 0, 1
- c. 1, 0
- d. 1, 1

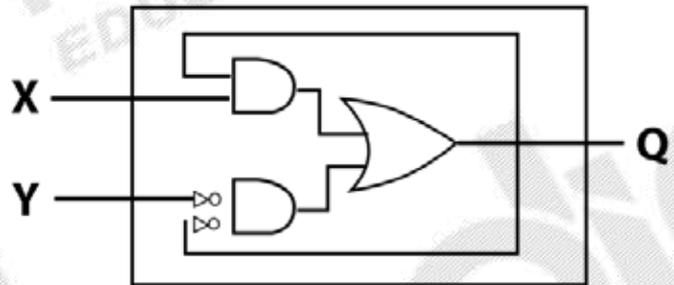

Q8. Consider the given XY flip-flop

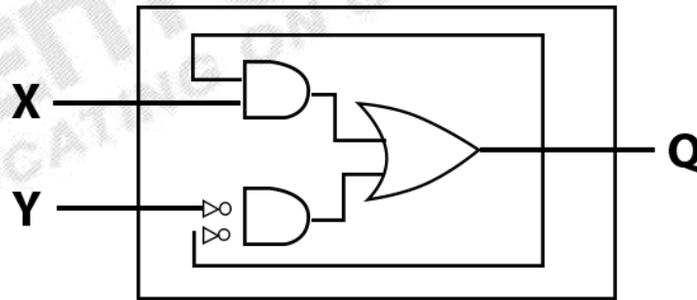

What are the values of X, Y respectively to change the state of flip flop from 1 to 0?

- a. 0, 0
- b. 0, 1
- c. 1, 0
- d. 1, 1

Q9. Number of 2×1 MUXes used in level 3 to construct a 64×1 MUX are _____ . Where the number of MUXes used gets reduced from level 1 to level N.

Q10. The minimum no of NOR gates required to implement the function $F = AB + A'B$

- a. 4
- b. 5
- c. 2
- d. 8

Q11. $F(A, B, C, D) = \sum m(1, 2, 3, \dots, 15)$. Simplified expression of the function F

- a. 1
- b. $A+B+C$
- c. $A+B+C+D'$
- d. $A+B+C+D$

Q12. Which gates do not follow the Associative law?

- a. AND Gate
- b. Universal Gate
- c. Ex-OR Gate
- d. None of these

Q13. Number of input conditions that will produce low output in an N input NOR Gate is?

- a. $2^N - 1$
- b. 1
- c. $2^N - N$
- d. N

Q14. A register contains 2' complement number 10100. When this register value is divided by 2 then the value at the o/p of register in decimal is?

Q15. Which of the given options is invalid

- a. 256 x 1 MUX
- b. 4 x 10 Decoder
- c. 7 x 256 decode
- d. 1 x 256 DEMUX

Q16. How many 2 I/P NAND gates required to recognize 2 I/P Ex-NOR gate?

- a. 3
- b. 4
- c. 5
- d. 6

Q17. How many 2 I/P NAND gates required to recognize full Subtractor?

Q18. Consider the following multiplication

$$(10w1z)_2 \times (15)_{10} = (y01011001)_2$$

Which one of the following gives appropriate values of w, y and z.

- a. $w=0, y=0, z=1$
- b. $w=0, y=1, z=1$
- c. $w=1, y=1, z=0$
- d. $w=1, y=1, z=1$

Q19. Simplify the given Boolean expression using the Boolean algebra properties:

$$v + v'w + v'w'x + v'w'x'y + v'w'x'y'z$$

- a. $v' + w + x + y + z$
- b. $v + w + x + y + z$
- c. $v' + w + x' + y + z$
- d. $v' + w' + x + y + z$

Q20. Convert $(1220212120)_3$ into $(?)_9$?

- a. 67765
- b. 56775
- c. 67756
- d. 56776

Q21. The negative decimal number $-N$ in the 2's complement representation is 1011. Then the representation for $-(N+1)$ is?

- a. 1100
- b. 1110
- c. 1010
- d. 1101

Q22. The switching expression corresponding to $f(A,B,C,D) = (1, 4, 5, 9, 11, 12)$ is

- a. $BC'D' + A'C'D + AB'D$
- b. $ABC' + ACD + B'C'D$
- c. $ACD' + A'B'C' + AC'D'$
- d. $A'BD + ACD' + BCD'$

Q23. Consider the following Boolean function of 4 variables $f(w, x, y, z) = (1, 3, 4, 6, 9, 11, 12, 14)$. The function is

- a. Independent of one variable
- b. Independent of two variables
- c. Independent of three variables
- d. Dependent on all the variables

Q24. How many number of prime-implicants for the given function $f(A, B, C, D) = \sum m(0, 2, 5, 6, 7)$

Q25. The minterm of $f(P, Q, R) = PQ + QR' + PR'$ is

- a. $m_2 + m_4 + m_6 + m_7$
- b. $m_0 + m_1 + m_6 + m_7$
- c. $m_0 + m_1 + m_3 + m_7$
- d. $m_2 + m_4 + m_5 + m_7$


Q26. If $x'y' = 0$, then $x \oplus y$ is

- a. $x + y$
- b. $x' + y'$
- c. $x + y'$
- d. $x' + y$

Q27.

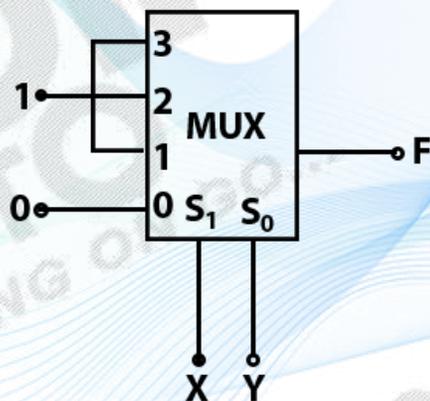- a. $(xy)' + x$
- b. $x + y$
- c. $x' + y'$
- d. $'xy + x$


The Output F of the 4-to-1 MUX shown in figure is



Q28. Consider the equation $(43)_x = (y3)_8$ where 'x' and 'y' are unknown. The number of possible solutions is _____.

- a. 3
- b. 4
- c. 5
- d. 6

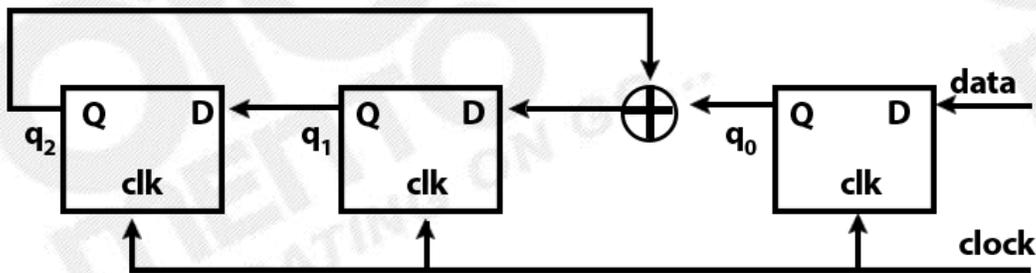
Q29. Consider the circuit in the diagram. The \oplus operator represents Ex-OR. The D flipflops are initialized to zeroes (cleared).



The following data: 100110000 is supplied to the “data” terminal in nine clock cycles. After that the values of q2 q1 q0 are:

- a. 000
- b. 001
- c. 010
- d. 101

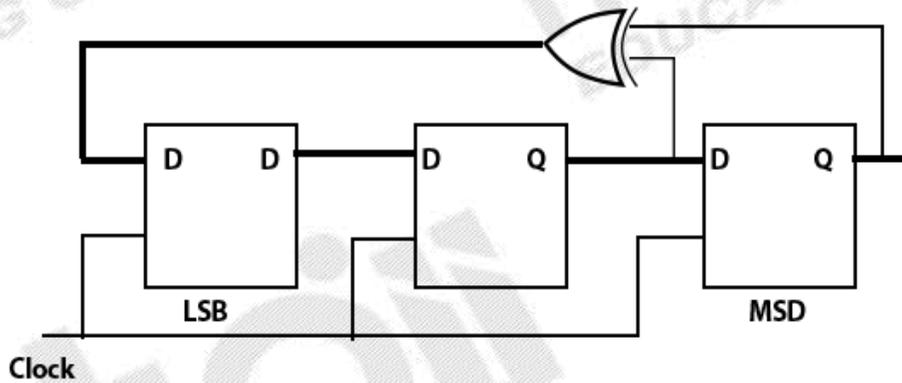Q30. Consider the circuit given below with initial state $Q_0 = 1, Q_1 = Q_2 = 0$. The state of the circuit is given by the value $4Q_2 + 2Q_1 + Q_0$. LSB output is denoted by Q_0 , and MSB output is denoted by Q_2 .




Which one of the following is the correct state sequence of the circuit?

- a. 1,3,4,6,7,5,2
- b. 1,2,5,3,7,6,4
- c. 1,2,7,3,5,6,4
- d. 1,6,5,7,2,3,4

Q31.

- a. 2 clock pulses
- b. 3 clock pulses
- c. 10 clock pulses
- d. 6 clock pulses

For the circuit shown below:

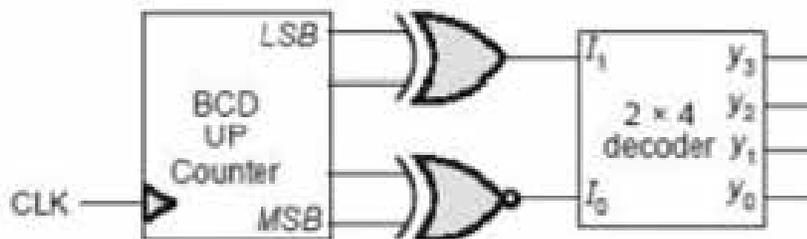


For how many number of clock pulses for which y_2 is '1' ?

Q32.

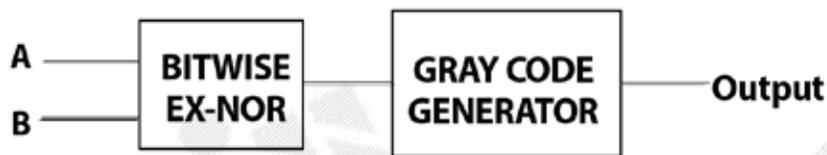- a. 251
- b. 253
- c. 254
- d. 255


For the circuit given below. If $A = 10101010$ and $B = 11111111$



What is the decimal equivalent of the output ?

Q33. Consider the digital circuit shown below

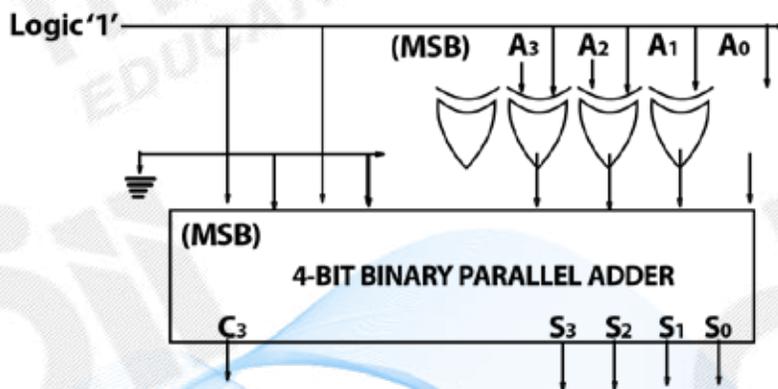
- a. 9's complement circuit
- b. 0's complement circuit



The digital circuit acts as

- c. 5's complement circuit
- d. 9's complement circuit if $C_3 = 0$ and 10's complement circuit if $C_3 = 1$.

Consider the logic circuit given below:

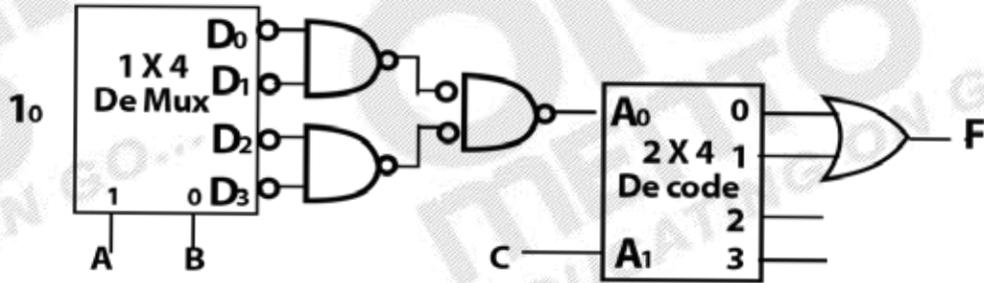

The minimized expression for F is

Q34.

- a. C'
- b. $/_0$
- c. C
- d. $/_0^1$

Q35. The Q-output of J-K flip-flop is 1. The output does not change when a clock pulse is applied. The input J and K will be respectively (x- don't care state)

- a. 0 and x
- b. 0 and 1
- c. 1 and 0
- d. x and 0

Q36. In a right shift register, right shift operation of binary 11 gives


- a. 5.5
- b. 5
- c. 6
- d. None of these

Q37.

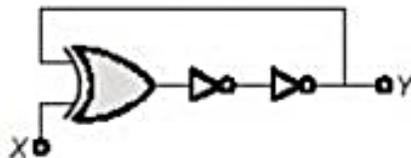- a. $X = 0$
- b. $X = 1$
- c. $X = 0$ or 1
- d. $X = Y$

All the logic gates in the circuit shown below have finite propagation delay.

The circuit can be used as a clock generator, if



Q38. X-Y flip flop, whose characteristics Table is given below is to be implement using a J-K flip flop
This can be done by making


- a. $J = Y', K = X$
- b. $J = Y, K = X'$
- c. $J = X, K = Y'$
- d. $J = X', K = Y$

X	Y	Q_{n+1}
0	0	1
0	1	Q'_{n+1}
1	0	Q_n
1	1	0

Q39.

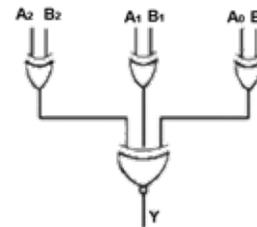- a. 010, 111
- b. 101, 110
- c. 010, 101
- d. 101, 011

A digital circuit which compares two numbers $A_2 A_1 A_0$ and $B_2 B_1 B_0$ shown in f



To obtain output $Y=1$, the valid combinat

Q40.

- a. $\Pi M(4, 6)$
- b. $\Sigma m(0, 1, 2, 3, 5, 7)$
- c. $\Sigma m(4, 6)$
- d. $\Pi M(0, 1, 2, 3, 5)$

boolean expression $f(x, y, z)$ in its canonical form he decoder is shown below is

